

**B. TECH.**  
**THEORY EXAMINATION (SEM-III) 2018-19**  
**NETWORK ANALYSIS AND SYNTHESIS**

Time : 3 Hours

Max. Marks : 100

Note: In case of numerical problem assume data wherever not provided.

**SECTION – A**

1 . Attempt all of the following questions:

10 x 2 = 20


- (a) Define planar graph?
- (b) State reciprocity theorem.
- (c) State two properties of the R-L driving point impedance function.
- (d) Write the equation of hybrid parameter.
- (e) What is duality?
- (f) Briefly describe the principle of Norton’s theorem.
- (g) What is application of transmission parameter?
- (h) Write down the properties of incidence matrix.
- (i) What is the required parameter of an ideal filter?
- (j) Defined cascade connection in two port network.

**SECTION – B**

2. Attempt any three of the following questions:

3 x 10 = 30

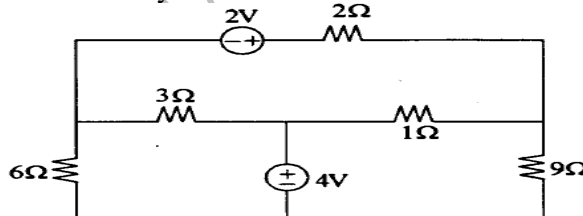- (a) Explain the Tellegen’s and verify it for the network shown.



- (b) Explain in detail with diagram the interconnection of two port network.
- (c) Derive the condition for symmetry and reciprocity for Z parameters.
- (d) Find the cauer forms of RL impedance functions

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$


- (e) State and proved Millman’s theorem.

**SECTION – C**

3. Attempt any one part.

1 x 10 = 10

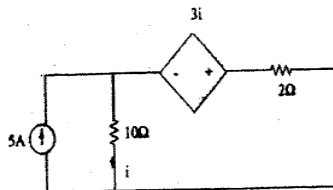- (a) Determine the Norton’s equivalent of the network shown in figure.



- (b) For the given network, draw the pole zero diagram and hence obtain the time response I(t).

$$I(s) = \frac{5s}{(s+1)(s^2 + 4s + 8)}$$

**4. Attempt any one part.**


**1 x 10 = 10**

- (a) State and proved the maximum power transfer theorem applied to the AC circuit.  
 (b) Test whether the polynomial P(s) Hurwitz or not.  
 (i)  $s^3 + 3s^2 + 2s$   
 (ii)  $s^4 + 5s^3 + 5s^2 + 4s + 10$ .

**5. Attempt any one part.**

**1 x 10 = 10**

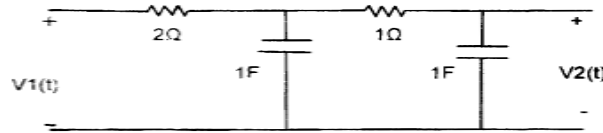- (a) Determine voltage transfer function  $V_2(s)/V_1(s)$  for the network shown in figure.




- (b) Write the necessary condition for driving point function and transfer function.

**6. Attempt any one part.**

**1 x 10 = 10**

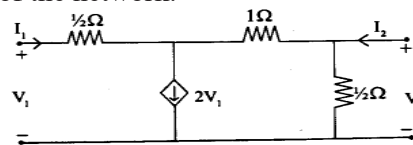- (a) Find the Y and Z parameter of the network.



- (b) Design a low pass filter both  $\pi$  and T network having a cut-off frequency of 1 KHz to operate with a terminated load resistance of 200Ω.

**7. Attempt any one part.**

**1 x 10 = 10**

- (a) Find the number of poles in the left half of s plane for a system whose characteristics equation is given is,

$$s^4 + 2s^3 + 3s^2 + 4s + 5 = 0$$

- (b) For the given reduce incidence matrix. Draw the graph and hence obtain the f-cutset matrix.

$$\begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$