

Paper Id

1	3	0	3	1	4
---	---	---	---	---	---

Roll No.

--	--	--	--	--	--	--	--	--	--

B. TECH
THEORY EXAMINATION (SEM-III) 2018-19
NETWORK ANALYSIS & SYNTHESIS

Time : 3 Hours

Max. Marks : 100

Note : Be precise in your answer. In case of numerical problem assume data wherever not provided

SECTION – A

1. Attempt all parts of the following questions:

2×10=20

- (a) With the help of mathematical expressions and characteristics curve, explain unit step and impulse signals used to analyse the network?
 (b) Draw Pole-Zero diagram for following impedance function:

$$Z(s) = \frac{(s + 1)}{(s^2 + 2s + 2)}$$


- (c) State initial value and final value theorem.
 (d) Explain the concept of transfer function.
 (e) State Thevenin's theorem.
 (f) What is the condition for reciprocity of z-parameter and h-parameter?
 (g) Describe the various elements of a network.
 (h) Define Positive real function.
 (i) What is unilateral Laplace transform? Give the condition for the existence of the Laplace transform.
 (j) Give the statement of superposition theorem.

SECTION B


2. Attempt any three parts of the following questions:

3×10=30

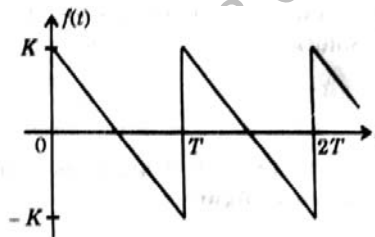- (a) Explain Convolution integral and convolution theorem.
 (b) Determine the Laplace transform of the waveform shown below: -



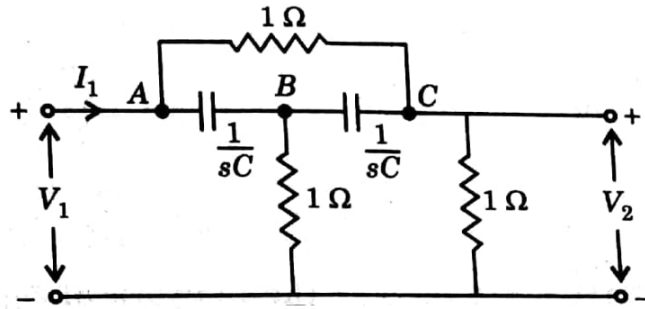- (c) What are two port networks? Explain various types of interconnections of two port network.
 (d) Find the driving point impedance $Z_{11}(s)$, transfer impedance $Z_{21}(s)$ and voltage transfer function $G_{12}(s)$ for the circuit shown in the figure below.




- (e) Write down the properties of Positive real function. Find if the function $Z(s) = \frac{2s^2+5}{s(s^2+1)}$ is positive real or not.

SECTION C

3. Attempt any one part of the following question: 1×10=10

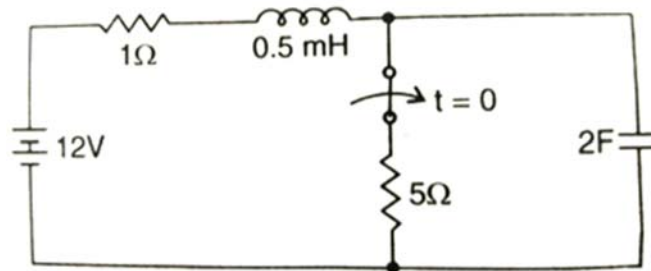- (a) The switch in the circuit of the given figure has been closed for a very long time. It opens at $t=0$.




Find $v_C(t)$ for $t > 0$ using differential equation approach.

- (b) Design first order high pass active filter and draw its frequency response.

4. Attempt any one part of the following question: 1×10=10

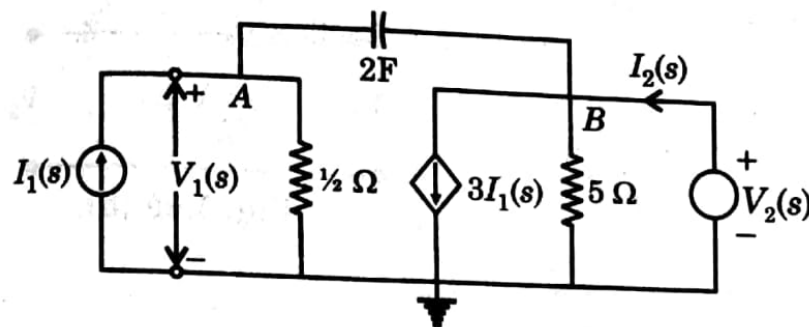- (a) Determine the h-parameters of the network given in the figure below:-



- (b) If $I(s) = \frac{s^2+5s+9}{s^3+5s^2+12s+8}$; find $i(t)$.

5. Attempt any one part of the following question:

1×10=10

(a) Find the range of values of “a” so that following function is a Hurwitz:

$$P(s) = s^4 + s^3 + as^2 + 2s + 3.$$

(b) What are active filters? List and explain types of active filters.

6. Attempt any one part of the following question:

1×10=10

(a) An impedance function is given by

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$


Find the R-C representation of (i) Foster I and (ii) Cauer I form.

(b) Synthesize $Y_{21}(s) = \frac{s^3}{s^3+3s^2+3s+2}$ with 1Ω termination.

7. Attempt any one part of the following question:

1×10=10

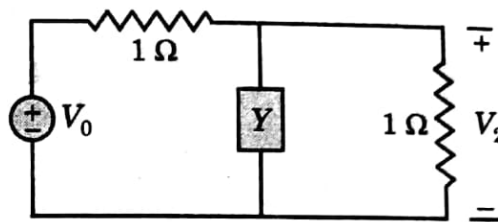
(a) What are the properties of R-L impedance function? For the network shown in the figure below: -



$$\frac{V_2}{V_0} = \frac{1}{2+Y} = \frac{s(s^2+3)}{2s^3+s^2+6s+1}$$

Synthesize Y as the L-C admittance.

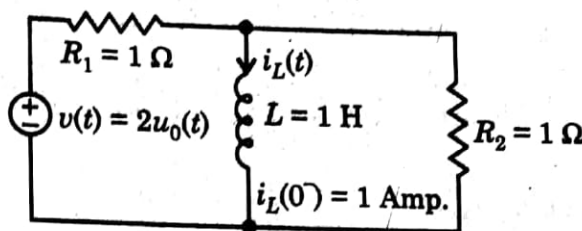(b) Construct transformed network of the circuit shown in the figure below.



Find out the Laplace transform function $I_{R_2}(s)$ and then using initial and final value theorems find out the initial and the final value of current $i_{R_2}(t)$, through R_2 . Verify the results by solving for $i_{R_2}(t)$.