

Paper Id:

130740

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.TECH.
(SEM VII) THEORY EXAMINATION 2019-20
VLSI DESIGN

Time: 3 Hours**Total Marks: 70****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2x7=14**

- a) What do you mean by Z_{pd} , Z_{pl} in the inverter circuit.
- b) Give the circuit arrangement for 2 input NOR gate using CMOS logic.
- c) What is parasitic delay.
- d) What is channel length modulation
- e) Implement 2:1 MUX using CMOS Transmission Gate.
- f) What are needs for low power VLSI chips.
- g) Write down the Applications of FPGA.

SECTION B**2. Attempt any three of the following:****7x3=21**

- (a) Explain the Fabrication Process of N-MOS transistor. Explain the MOSFET capacitance with suitable sketch.
- (b) Derive the expression for V_{IH} , V_{IL} , NM_L , and NM_H for CMOS inverter.
- (c) Explain Domino and NORA CMOS logic circuit with suitable example.
- (d) Write short note on DRAM cell. Explain leakage and refresh operation in DRAM cells.
- (e) Explain the following:
 - (i) Scan Based Technique.
 - (ii) Fault types and models.

SECTION C**3. Attempt any one part of the following:****7x1=7**

- (a) Discuss the hierarchy of various semiconductors with Moore's law. Draw the Y- chart and explain the VLSI design process.
- (b) Implement the Boolean function $Z = AB + (C + D)(E + F) + GH$ using standard CMOS and Domino CMOS logic.

4. Attempt any one part of the following:**7x1=7**

- (a) Why transistor scaling is of great importance in VLSI? Write down comparison between Constant field scaling and Constant voltage scaling.
- (b) (i) Explain the concept of RC Delay model.
(ii) What are the limitations of logical effort.

5. Attempt any one part of the following:**7x1=7**

- (a) Draw the circuit diagram of SRAM and explain read and write operation.
- (b) Explain various types of power dissipation in CMOS circuits.

6. Attempt any one part of the following:**7x1=7**

- (a) Write the Difference between Dynamic CMOS logic circuit and Static CMOS logic circuit. Explain the classification of Dynamic CMOS logic circuit and design a 2 input EXOR logic Gate using Domino logic.
- (b) Describe the working of three stage pseudo nMOS dynamic shift register driven with two-phase clocking giving its circuit.

7. Attempt any one part of the following:**7x1=7**

- (a) Write a short note on Built-in-self test (BIST) techniques.
- (b) Briefly explain variable threshold CMOS (VTCMOS) circuit.