

BTECH
(SEM III) THEORY EXAMINATION 2021-22
NETWORK ANALYSIS AND SYNTHESIS

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.

2 x 10 = 20

- a. Illustrate the admittance parameter of a two-port network.
- b. Describe the band stop filter with suitable example.
- c. Demonstrate time scaling property of Laplace transform.
- d. Describe the singularity function with suitable example.
- e. Demonstrate time convolution property of Fourier transform.
- f. Illustrate the drawback of Fourier Transform and how this drawback can be removed by using Laplace transform.
- g. Describe and state Thevenin's theorem with suitable example.
- h. Describe the following terms for a network: Graph, Tree, Co-Tree, and Twig.
- i. Use source transformation to solve v_o in the circuit shown in figure 1.

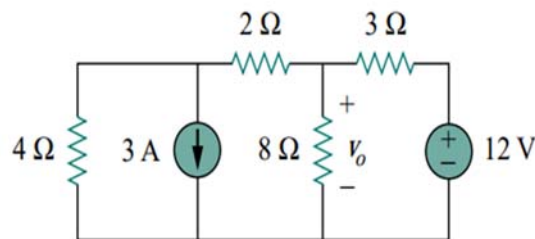


Figure 1

- j. When the voltage across a resistor is 120 V, the current through it is 2.5 mA. Calculate its conductance.

SECTION B

2. Attempt any three of the following:

10 x 3 = 30

- a. Identify the node voltages in the circuit shown in figure 2.

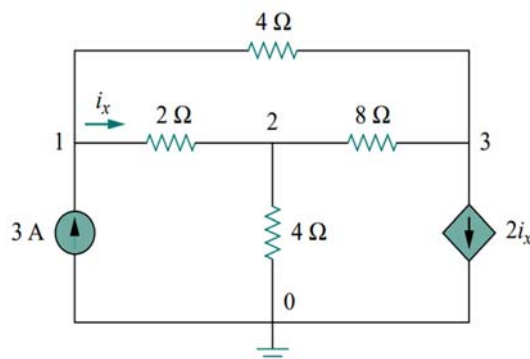


Figure 2

