

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.TECH.
(SEM VII) THEORY EXAMINATION 2022-23
VLSI DESIGN

*Time: 3 Hours**Total Marks: 100***Note:** Attempt all Sections. If you require any missing data, then choose suitably.**SECTION A****1. Attempt all questions in brief. 2x10 = 20**

- (a) Define the term worst case timing analysis.
- (b) State the term delay.
- (c) Define the term lumped circuit.
- (d) What is a transient response in any circuit?
- (e) What is a dynamic circuit?
- (f) Differentiate between Combinational and Sequential circuits.
- (g) What is a volatile memory?
- (h) Define the term Power consumption.
- (i) Define the term faults.
- (j) What is the term controllability?

SECTION B**2. Attempt any three of the following: 10x3 = 30**

- (a) Describe different propagation delays in VLSI Design.
- (b) Explain Skin effect and its related functions used in VLSI Design.
- (c) What is charge sharing VLSI? Define the solution to avoid or lessen charge sharing in any circuit.
- (d) Elaborate the pipeline architecture.
- (e) Define the term functional modeling in VLSI circuits.

SECTION C**3. Attempt any one part of the following: 10x1 = 10**

- (a) Describe different packaging techniques used in VLSI Circuits.
- (b) Elaborate general VLSI design flow by describing each block separately.

4. Attempt any one part of the following: 10 x1 = 10

- (a) Describe the term Logical effort and calculate the logical effort of a path.
- (b) Explain the distributed R-C model.

5. Attempt any one part of the following: 10x1 = 10

- (a) Describe the working and application of two-phase clocking systems.
- (b) Elaborate the working and applications np-CMOS logic.

6. Attempt any *one* part of the following: 10x1 = 10
- (a) Explain the working and applications of a Flash memory cell.
 - (b) Illustrate different types of RAM cells.
7. Attempt any *one* part of the following: 10x1 = 10
- (a) Describe different faults defined in any VLSI circuits.
 - (b) Explain the Built-in-Self-Test technique for testing a VLSI Circuit.

QP23DP1_082

| 17-01-2023 13:54:13 | 103.93.113.234